



F.E. (Semester – II) (RC 2016-17) Examination, May/June 2018
FUNDAMENTALS OF ELECTRONICS AND TELECOMMUNICATION
ENGINEERING


Duration : 3 Hours

Total Marks : 100

- Instructions :** 1) Answer **five** questions atleast **two** from Part **A**, **two** from Part **B** and **one** from Part **C**.
2) Assume suitable data if **necessary**.
3) Figures to the **right** indicate **full** marks.


PART – A

Answer **any two** full questions.

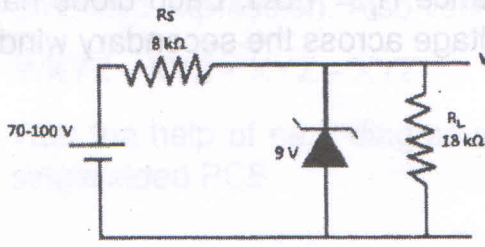
1. a) With the help of a neat diagram, explain the formation of a depletion region in a pn junction under the forward bias condition. 5
b) Differentiate between npn and pnp transistor. 2
c) Find the maximum and minimum values of the current through the zener diode for the following circuit. 5
- 
- d) Obtain the expression for ripple factor and rectification efficiency of a full wave rectifier. 8
 2. a) Draw and explain the output characteristics of a pnp transistor in CE configuration. Also mark the three regions of operation. 6
b) What is the effect of increase in V_{CB} on I_E , when V_{EB} is kept constant for pnp transistor in CB configuration. Explain. 2



 - c) Explain the working a p-channel junction field effect transistor. Also draw the drain and transfer characteristics. 6
- d) Using Thevenin's theorem, find the coordinates of the operating point for the circuit shown below. 6



 3. a) Explain the working of a bridge rectifier. 4
- b) Explain the construction and working of a p-channel depletion type MOSFET. 6
- c) What is the significance PIV of a diode ? Explain how PIV is measured for a full wave and bridge rectifier. 5
- d) In a half wave rectifier, the load resistance $R_L = 1.5\Omega$. Each diode has a forward bias resistance of 15Ω . The voltage across the secondary winding is $200 \sin 314t$. Find
- Peak value of current
 - Average value of current
 - Rms value of current
 - Ripple factor
 - Rectification efficiency.



PART – B

Answer **any two full** questions.

4. a) Implement the following gates using only NAND gate. 4
- OR gate
 - XOR gate



- b) Explain the symbol, construction and operation of a silicon controlled rectifier. 8
- c) Explain the functions of transmitter and receiver block of an electronic communication system. 4
- d) With the help of a block diagram, explain the basic parts of a microcontroller. 4
5. a) Write distributive law, associative law and commutative law and verify using truth table. 6
- b) Two square waves, A of frequency 200 kHz and B of frequency 400 kHz are applied as inputs to the logic gates. Draw the output waveform in each case. 4
- i) NAND gate
- ii) NOR gate
- c) Explain the need for modulation. Mention the different modulation methods. 4
- d) Draw a neat diagram and input-output waveforms of an inverting operational amplifier. Also obtain the expression for closed loop gain. 6
6. a) What is a strain gauge ? Explain the importance of gauge factor of the strain gauge. 4
- b) Draw and explain the block diagram of programmable logic controller. 5
- c) Reduce the following Boolean expression and draw the logic diagram of the simplified expression. Also verify using the truth table 5
- $\overline{W}XY\overline{Z} + XY\overline{Z} + X\overline{Y}\overline{Z} + X\overline{Y}Z$
- d) With the help of neat diagrams, explain the procedure of fabrication of a single sided PCB. 6

PART – C

Answer **any one full** question.

7. a) With the help of a neat diagram, differentiate between depletion and enhancement types MOSFET. 4
- b) Explain the avalanche and zener breakdown mechanism in a pn junction diode. 5
- c) Explain the working of a zener diode as a voltage regulator. 6
- d) Explain the construction and operation of a CMOS inverter. 5



8. a) With the help of neat diagrams classify the solid materials on the basis of conductivity and energy band diagram. 6
- b) What is positive logic and negative logic ? 6
- c) Using the Boolean laws, prove the following. 4
- i) $\bar{X}Y + X + \bar{Y}X = Y + X$
- ii) $\left[\bar{X}Y + (X + Y) \right] . XY = X\bar{Y}$
- d) The input characteristics of a transistor are given in figure below. Determine the dynamic input resistance of the transistor at point P where $V_{CB} = 4V$. Also mention the type and configuration of the transistor. 4

