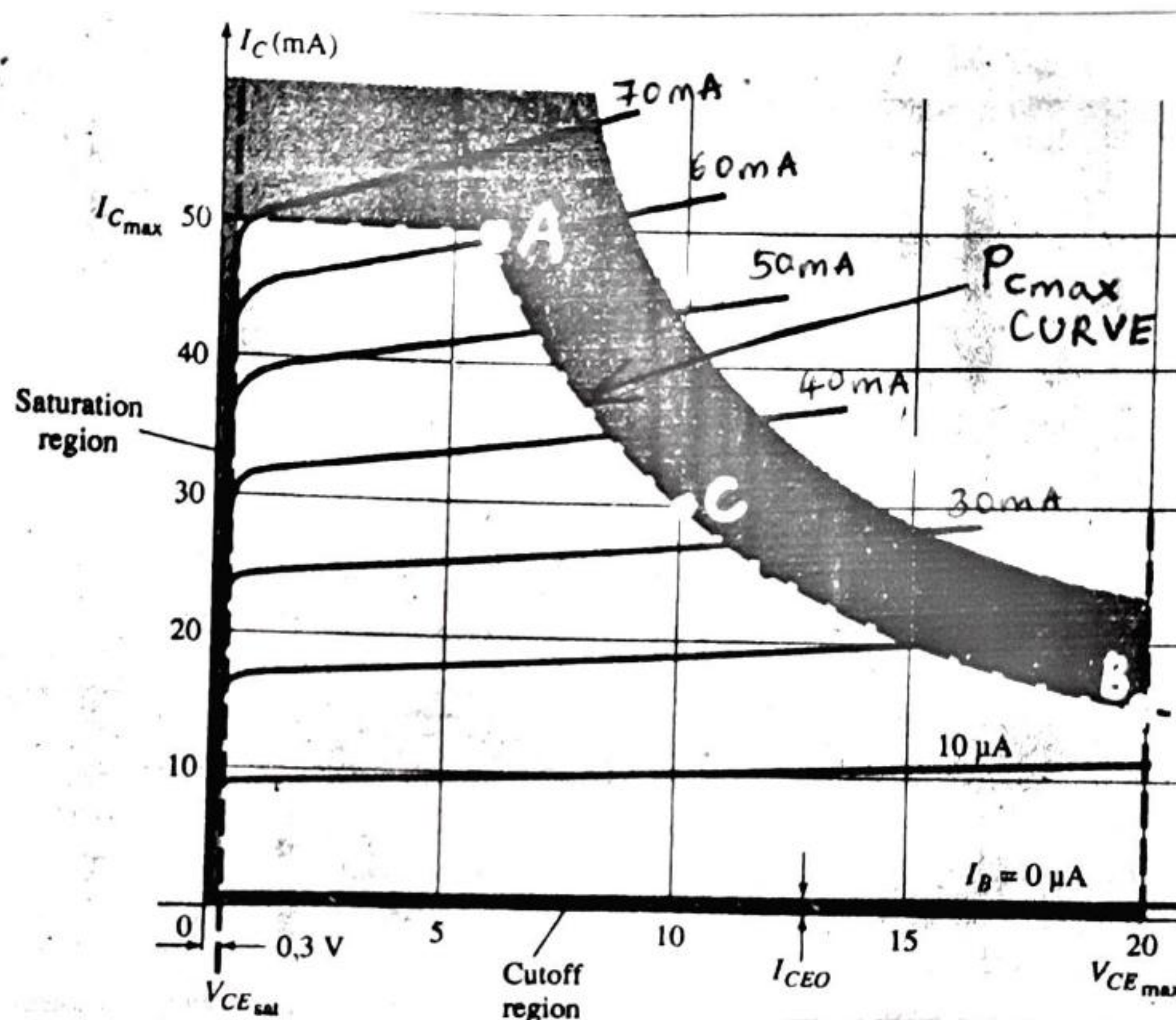


★

## LIMITS OF OPERATION

Why limits are needed?

For each transistor, there is a region of operation on the characteristics. Operation in this region will ensure that max. ratings are not being exceeded & the output signal exhibits minimum distortion.



The limits of operation are:

- (1) Maximum collector current ( $I_{Cmax}$ )
- (2) Maximum collector-to-emitter voltage ( $V_{CEmax}$ )
- (3)  $V_{CEsat}$ : It is the minimum  $V_{CE}$  that can be applied without the transistor going into the non-linear region (saturation region). It is defined by a vertical line on the characteristics (usually 0.3V).
- (4) Cut-off Region: It is defined as the region below  $I_C = I_{CEO}$ . This region must be avoided if o/p signal is to have minimum distortion.
- (5)  $P_{Cmax}$ : This is the max power dissipation level given by  $P_{Cmax} = V_{CE} I_C$

Note: For CB Configuration  $P_{Cmax} = V_{CB} I_C$



Operating in the resulting region of the figure will ensure:

- i) Minimum distortion of o/p signal.
- ii) Current & voltage levels that will not damage device.

If the characteristic curves are unavailable or are not specified, be sure that  $I_C$ ,  $V_{CE}$  &  $(V_{CE} \cdot I_C)$  fall into the following range:

$I_{CE0} \leq I_C \leq I_{Cmax}$
$V_{CEsat} \leq V_{CE} \leq V_{CEmax}$
$V_{CE} I_C \leq P_{Cmax}$

★★ NOTE → The Power dissipation curve is plotted as follows:-

Suppose  $P_{Cmax} = 300 \text{ mW}$ .

At any point on the characteristics, the product of  $V_{CE}$  and  $I_C$  should not exceed  $300 \text{ mW}$ .

If we choose  $I_C = 50 \text{ mA}$

$$V_{CE} I_C = 300 \text{ mW}$$

$$\therefore V_{CE} = \frac{300 \text{ mW}}{50 \text{ mA}} = 6 \text{ V} \quad (\text{This is point A})$$

(See fig)

If we choose  $V_{CE} = 20 \text{ V}$

$$V_{CE} I_C = 300 \text{ mW}$$

$$\therefore I_C = \frac{300 \text{ mW}}{20 \text{ V}} = 15 \text{ mA} \quad (\text{This is point B})$$

Now say  $I_C = 25 \text{ mA}$

$$V_{CE} = \frac{300 \text{ mW}}{25 \text{ mA}} = 12 \text{ V} \quad (\text{This is point C})$$

∴ A Rough estimate of the Power dissipation curve can be drawn as shown in the fig.



Problems.

- 1) For a certain transistor,  $I_C = 6.25 \text{ mA}$ ,  $I_B = 100 \mu\text{A}$ . & collector to base leakage current is  $5 \mu\text{A}$ . Determine emitter current &  $\alpha_{dc}$ .

Sol<sup>n</sup> :  $I_C = 6.25 \text{ mA}$ ,  $I_B = 100 \mu\text{A}$ ,  $I_{CBO} = 5 \mu\text{A}$ .

$$I_E = I_B + I_C = 100 \mu\text{A} + 6.25 \text{ mA} = 6.35 \text{ mA}$$

$$I_C = \alpha_{dc} I_E + I_{CBO}$$

$$\therefore \alpha_{dc} = \frac{I_C - I_{CBO}}{I_E} = 0.9835$$

- 2) When emitter current of a transistor is changed by  $1 \text{ mA}$ , its collector current changes by  $0.995 \text{ mA}$ .

Calculate : (i) its CB short ckt current gain  $\alpha$

(ii) its CE short ckt current gain  $\beta$ .

Sol<sup>n</sup> :  $\alpha_{ac} = \frac{\Delta I_C}{\Delta I_E} = \frac{0.995 \times 10^{-3}}{1 \times 10^{-3}} = 0.995$

$$\beta_{ac} = \frac{\Delta I_C}{\Delta I_B} \quad \underline{\text{OR}} \quad \beta = \frac{\alpha}{1 - \alpha} = \frac{0.995}{1 - 0.995} = 199$$

- 3) Determine Emitter Current  $I_E$  for a transistor if  $I_B = 40 \mu\text{A}$  &  $\alpha_{dc} = 0.98$ .

Sol<sup>n</sup> :  $I_E = \frac{1}{(1 - \alpha_{dc})} I_B$  (CC Configuration)

$$= \frac{1}{(1 - 0.98)} \times 40 \mu\text{A}$$

$$= 2 \text{ mA}$$