

Total No. of Printed Pages:03

F.E Semester-I (Revised Course 2019-20)
EXAMINATION AUGUST 2020
Basics of Electrical & Electronics Engineering

[Duration : Two Hours]


[Total Marks : 60]

Instruction:


Answer THREE FULL QUESTIONS with ONE QUESTION FROM EACH
 PART

Part-A

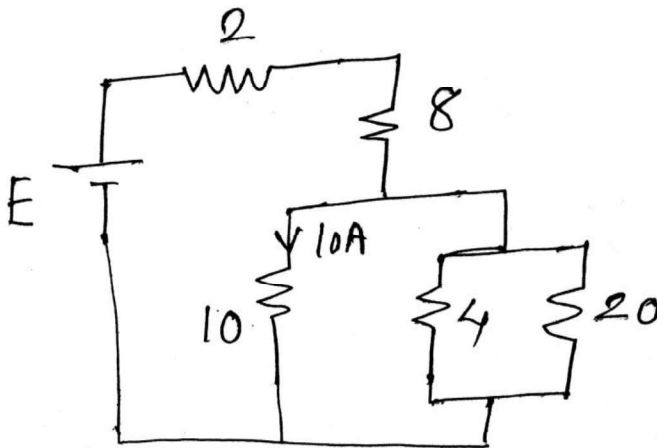- Q.1 a) What do you mean by Renewable energy sources? What are their advantages and restrictions? **10**
- b) In the circuit below find currents in all other resistors if current in 10Ω is $10A$. Hence find value of E **10**



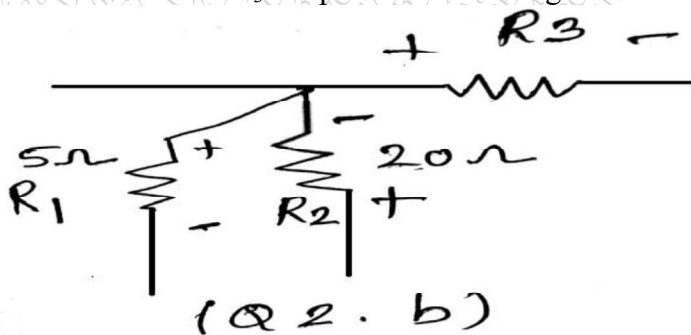- Q.2 a) Explain Kirchoff's laws with proper examples. **8**
- b) IF the voltages across R_1, R_2, R_3 are $20V, 40V, \& 60V$ respectively in the part of circuit shown. Find R_3 the polarities of voltages are as shown. **8**




- c) If a resistor ' R ' is carrying current I show that power dissipated is $\frac{V^2}{R} W$ where $V =$ voltage across the resistor. **4**

- Q.3 a) Define 'RMS' value of an waveform **4**

- b) Find RMS value of wave form

$$V(Q) = V_m \sin Q$$

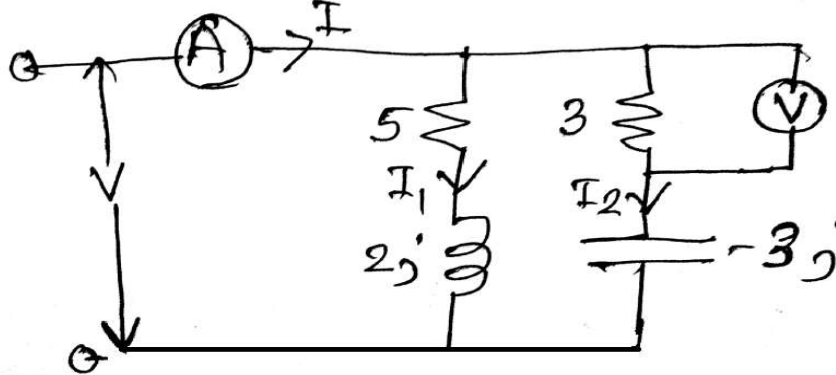- c) Find the reading of Ammeter if voltmeter reads 45V in the following circuit Also find I_1, I_2 and V and Draw phasor diagram




Part- B

- Q.4 a) Explain how zener diode may be used as voltage regulator. Draw its V-I characteristics indicating typical parameters. 8
- b) Explain output characteristics of transistor in CE configuration sketch them neatly with relevant circuit to obtain them in the laboratory. 8
- c) Draw neat circuit of full wave bridge rectifier and draw relevant wave forms. 4
- Q.5 a) Explain with neat circuits following biasing circuits of an transistor 10
- i) Fixed bias
- ii) Voltage divider bias
- b) Explain construction and V-I characteristics of SCR. How it can be used to control the phase of applied voltage. 10
- Q.6 a) Explain working of n-channel JFET and draw its $V_{DS} - i_D$ characteristics and explain it 8
- b) Explain working of depletion type and enhancement type MOSFET with neat operational sketches 12

Part- C

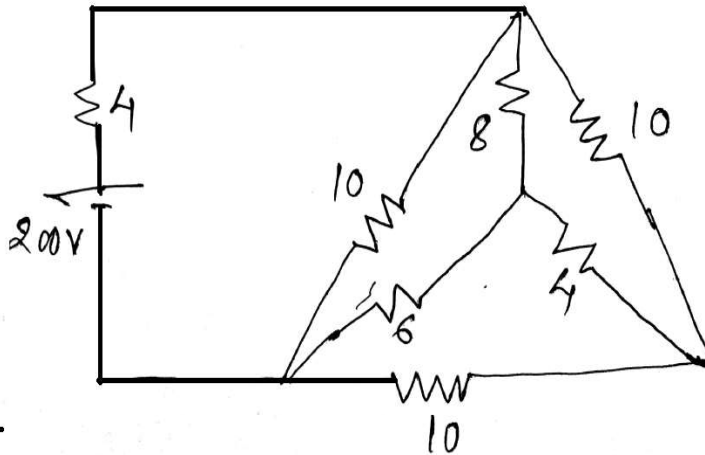- Q.7 a) Derive emf equation of an single phase transformer 8
- b) Draw neat phasor representation of 3- ϕ supply system and write expressions for 3 phases. 6
- c) Use star – delta transformation to find current I 6



- Q.8
- Explain following terms for transistor 8
 - Saturation and cut off regions
 - α and β current gains
 - Quiescent point
 - Power dissipation limit
 - What do you mean by power factor what is its significance in ac circuit 6
 - Explain working of LED 6