

Total No. of Printed Pages:4

F.E. (Sem - I) (Revised Course 2016-17)
EXAMINATION MAY/JUNE 2019
Fundamental Of Electrical Engineering

[Duration : 3 Hours]


[Max. Marks : 100]

Please check whether you have got the right question paper.


Instructions: Answer any two from each of Part A & B and one from Part C.

Part- A

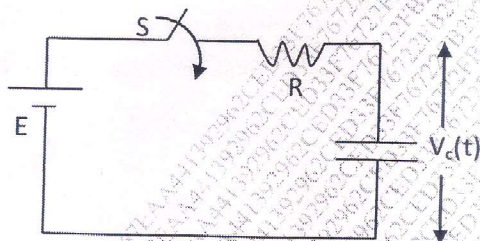
- Q.1
- a) Explain construction and working of thermal power plant with block diagram. 08
- b) In the following capacitor charging circuit, show that, $V_c(t)$ is $V_c(t) = E(1 - e^{-t/RC})$ after switch S is closed at $t=0$ 08



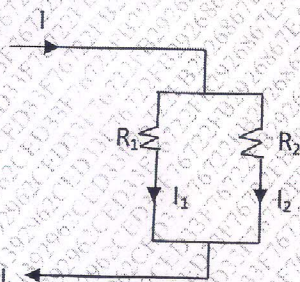- c) Find expression for currents I_1 & I_2 . 04




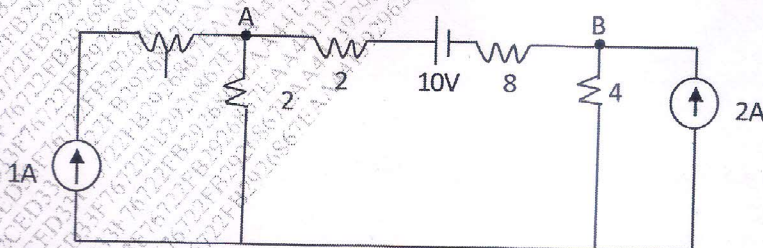- Q.2
- a) Find voltages of nodes A & B in the following circuit using nodal analysis. 08



- b) Use Norton's theorem to find current in galvanometer. Take $r_g = 2\Omega$.

08

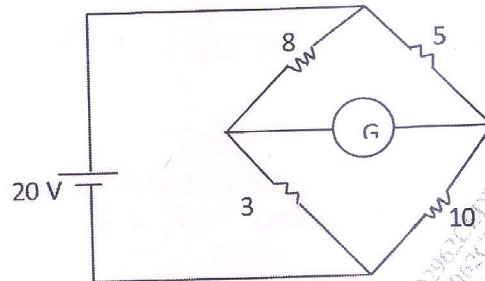


- c) Give the analogy between electrical and magnetic circuit.

04

Q.3

- a) Use Ampere's Law to get magnetic field of a long solenoid having N turns, L as length and ϕ as cross section area. Hence find its inductance.
- b) State and prove maximum power transfer theorem. Find the value of R_L and maximum power in the following circuit.

06

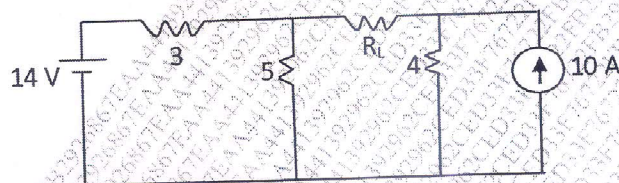

- c) Explain what you mean by coupling-coefficient.


04

Part-B

Q.4

- a) Find the rms and average value of the following waveform.

08

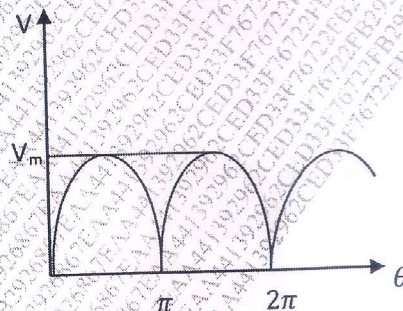

- b) Define what is power factor. What is p.f of following?


06

- 1) Pure resistor
- 2) Pure capacitor and pure inductor
- 3) Inductive circuit

4) Capacitive circuit

- c) Find the impedance Z_{AB} of the following circuit. Hence find I

06

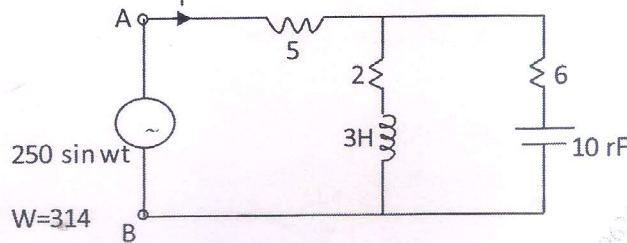


Q.5

- a) Derive relation between line voltage and phase voltage in star connected 3ϕ system. Draw neat circuit and phasor diagram.

06

- b) A voltmeter placed as shown reads 45V. What is the ammeter reading?

06

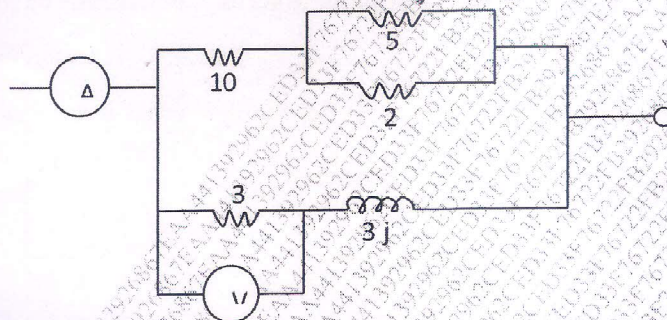

- c) An circuit draws current of $I = 3-4j$ when voltage $V = 100 \angle 30^\circ$ is applied to it. Find impedance of the circuit and active and reactive power drawn. What is the power factor of the circuit?

08


Q.6

- a) What is the purpose of an transformer derive emf equation of the transformer.

06

- b) A delta connected load of $5+8j$ is connected to 440V, 50Hz, 3ϕ system find line and phase currents.

08

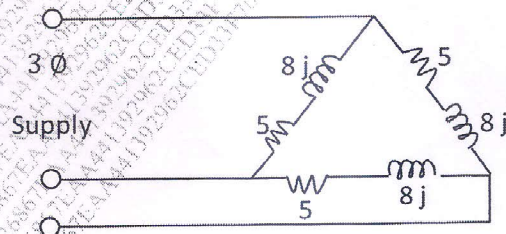

- c) Show that 3ϕ power measurement is possible using 2 Wattmeter's.


06

Part- C

Q.7

- a) Use superposition theorem to find current in 5Ω resistor below.

08

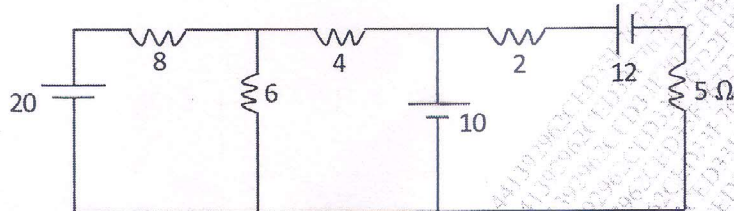

- b) What is the purpose of no-load and SC test on transformer. Draw neat circuits to perform these tests.

08


- c) What do you understand by phase sequence of 3ϕ supply? What is its significance?

04

Q.8

- a) Using the venin's theorem find current in 8Ω below.

08

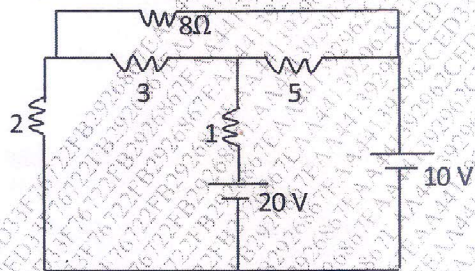

- b) Explain different components of Solar-PV power plant.

06

- c) Derive condition of maximum efficiency of transformer.

00