

ZENER DIODE AS VOLTAGE REGULATOR

- After the ripples have been smoothed or filtered from the rectifier o/p, we get a sufficiently steady d.c o/p.
- The problem with this d.c o/p voltage is that it varies with the i/p a.c voltage or load.
i.e If the input voltage increases, the d.c o/p voltage also increases & if load current increases, the o/p d.c voltage falls.
- In many applications we need a fixed o/p voltage regardless of the changes in the i/p voltage or load.
- Thus to improve the constancy of the d.c o/p voltage a voltage regulator circuit is used.
- Zener diode can be used as voltage regulator to provide a const. voltage. The simplest ckt is as shown below:

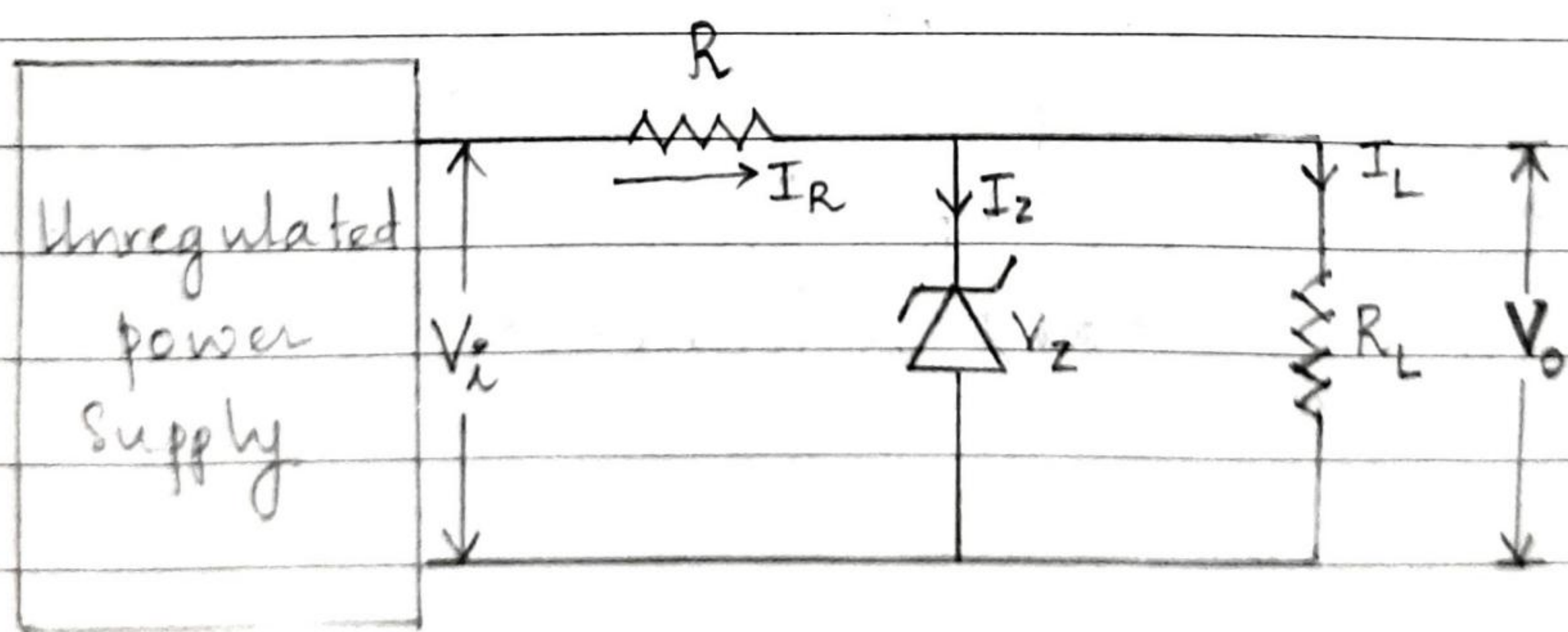


Fig: Zener-Diode Voltage Regulator circuit.

- The regulator ckt consists of a resistor R connected in series with input voltage & a zener diode connected in parallel with the load. The zener diode is selected in such a way that its breakdown voltage is equal to the desired regulating output.
- Zener diode will maintain constant voltage $V_Z = V_o$ across the load as long as i/p voltage is above V_Z .
- The current from the power supply splits at the jⁿ
 $\therefore \boxed{I_R = I_Z + I_L}$

R_L FIXED, V_i VARIES:

- Suppose i/p voltage V_i increases, the excess voltage is dropped across R & the current I_R increases. This increases the current through zener I_Z (I_L cannot change since R_L is fixed). Thus total current is balanced & load current remains constant. $\therefore V_o$ remains constant.
- Suppose i/p voltage V_i decreases, voltage drop across R is reduced, I_R decreases and I_Z also falls. Because of the self adjusting voltage drop across R , the o/p V_o fluctuates to a much lesser extent.

V_i FIXED, R_L VARIES:

- Suppose R_L increases, load current I_L decreases, the zener diode passes extra current so that I_R is kept constant (since V_i is constant). The output voltage of the circuit is thus stabilized.
- Suppose R_L decreases, I_L increases, the current I_Z falls by the same percentage in order to maintain constant current I_R . So that voltage drop across R remains constant & hence V_o remains constant.

Thus 3 conditions can be considered:

- ① Fixed Supply & Load
- ② Fixed Supply & Variable Load
- ③ Fixed Load & Variable Supply

① V_i & R_L FIXED

A Simple Zener diode regulator is shown: - (fig(a))

The applied d.c voltage is fixed & so is the load resistor.

The analysis can be broken down into 2 steps:


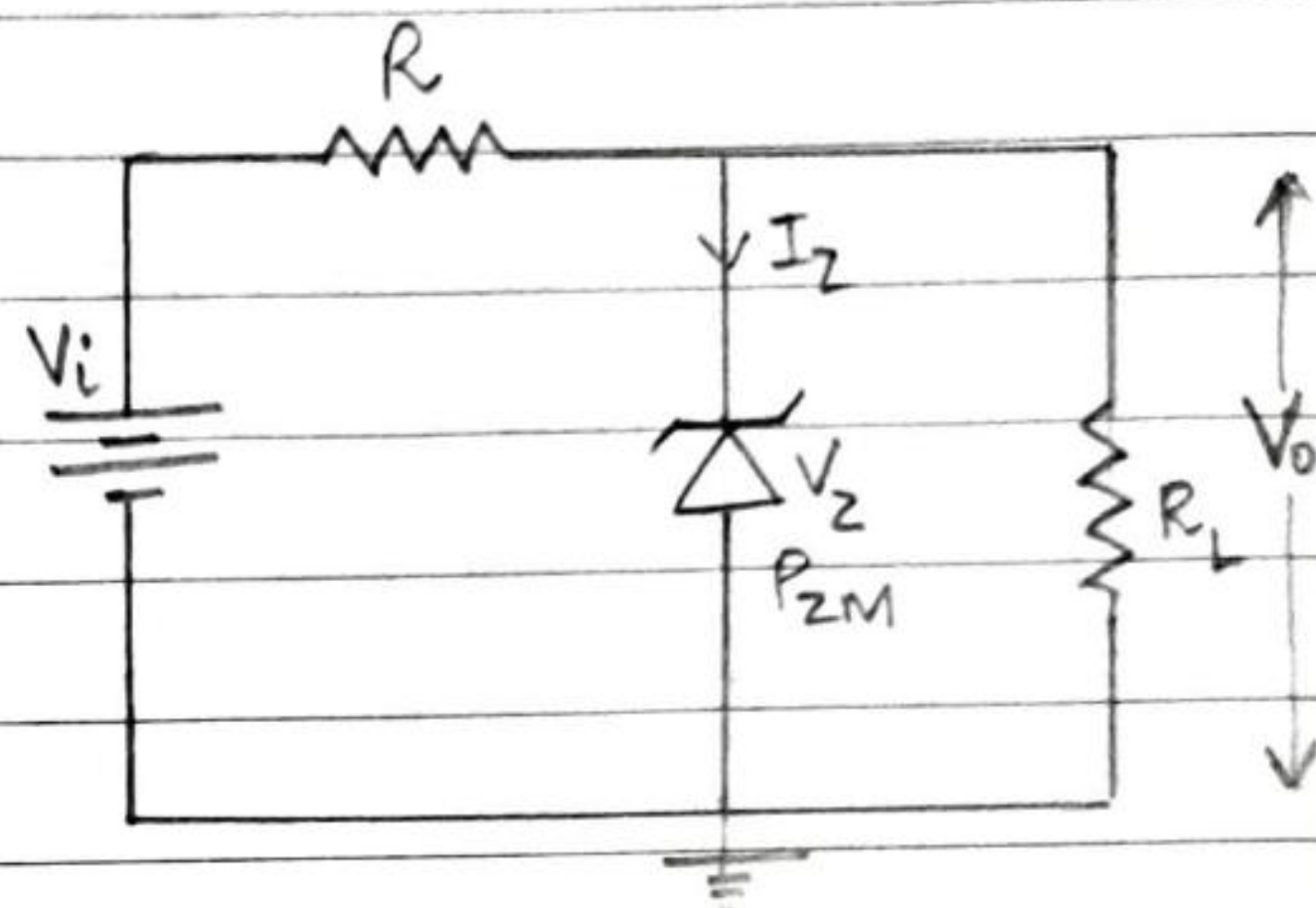


fig (a)

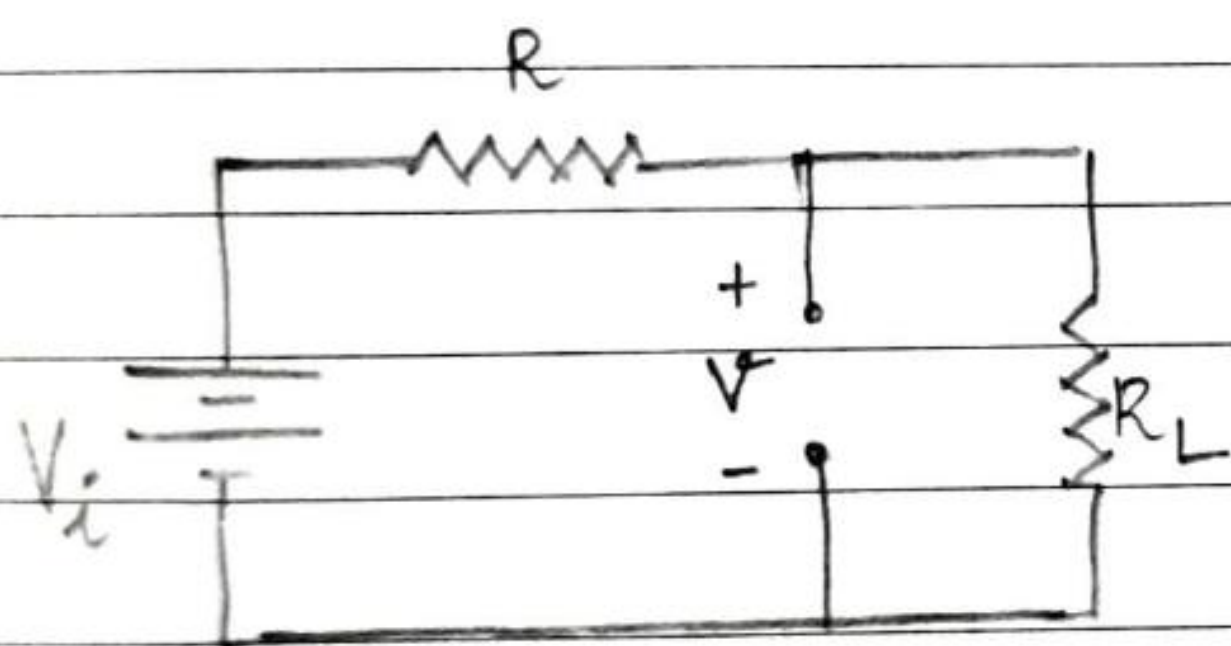Step 1: Determine the state of the Zener diode by calculating the voltage across it. i.e. Apply Voltage Divider Rule.



fig(b)

i.e. find V (fig(b))

$$V = \frac{V_i \times R_L}{R + R_L} (= V_L)$$

If $V \geq V_z$, Zener diode is ON

If $V < V_z$, diode is off \therefore Open ckt.


Step 2: Substitute the appropriate equivalent ckt & solve for the desired unknowns.

If $V \geq V_z$, ckt can be drawn as in fig(c).

Here $V_L = V_z$

$$I_R = I_z + I_L$$

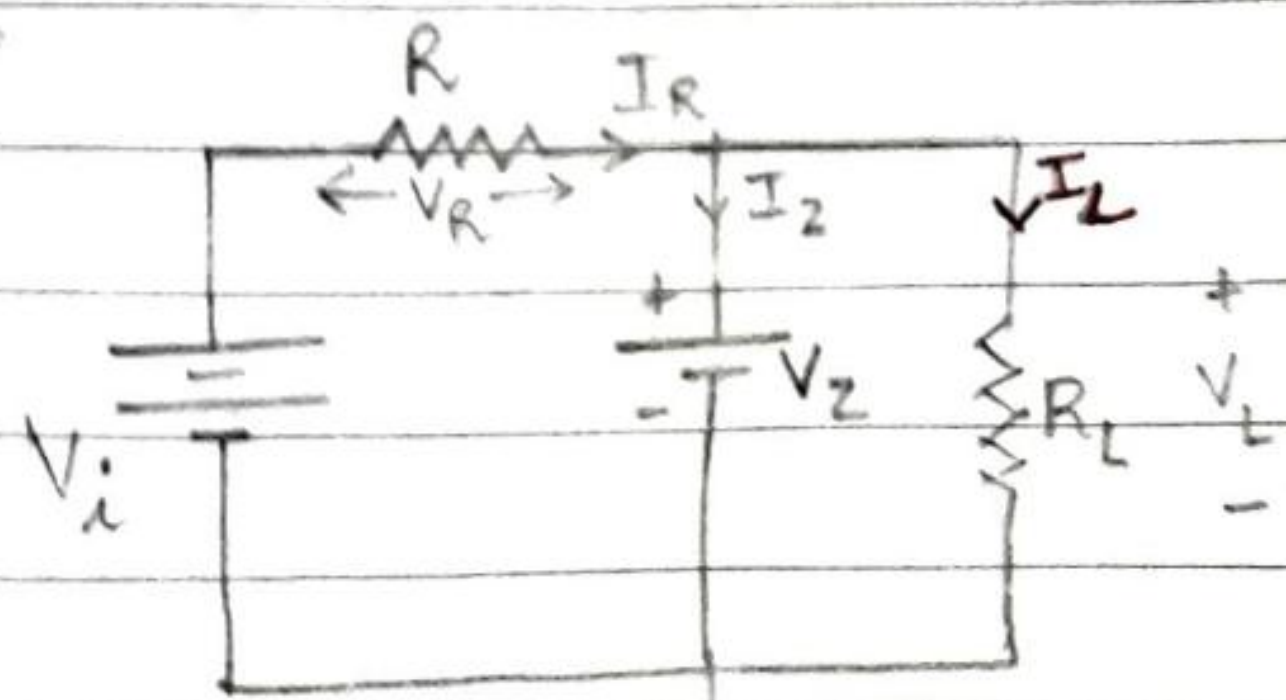where $I_L = \frac{V_L}{R_L}$ & $I_R = \frac{V_R}{R} = \frac{V_i - V_z}{R}$



fig(c)


The power dissipated by Zener is given by $P_z = V_z I_z$

\downarrow
This must be less than P_{zM}

Q. For zener diode of the given network, determine:

(a) V_L , V_R , I_Z & P_Z


(b) Repeat with $R_L = 3k\Omega$.

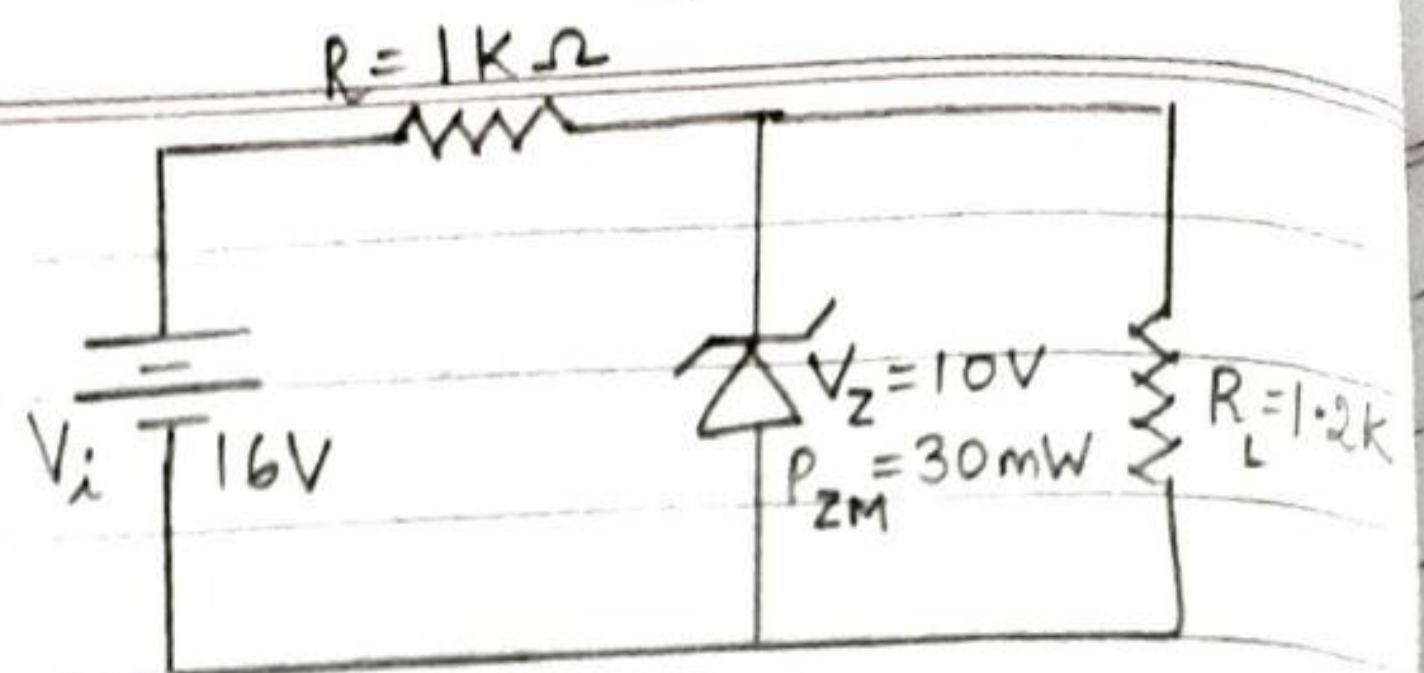

Soln:- Determine the state of zener:

$$V = \frac{V_i \times R_L}{R_L + R} = \frac{16 \times 1.2k\Omega}{1.2k\Omega + 1k\Omega} = 8.73V$$

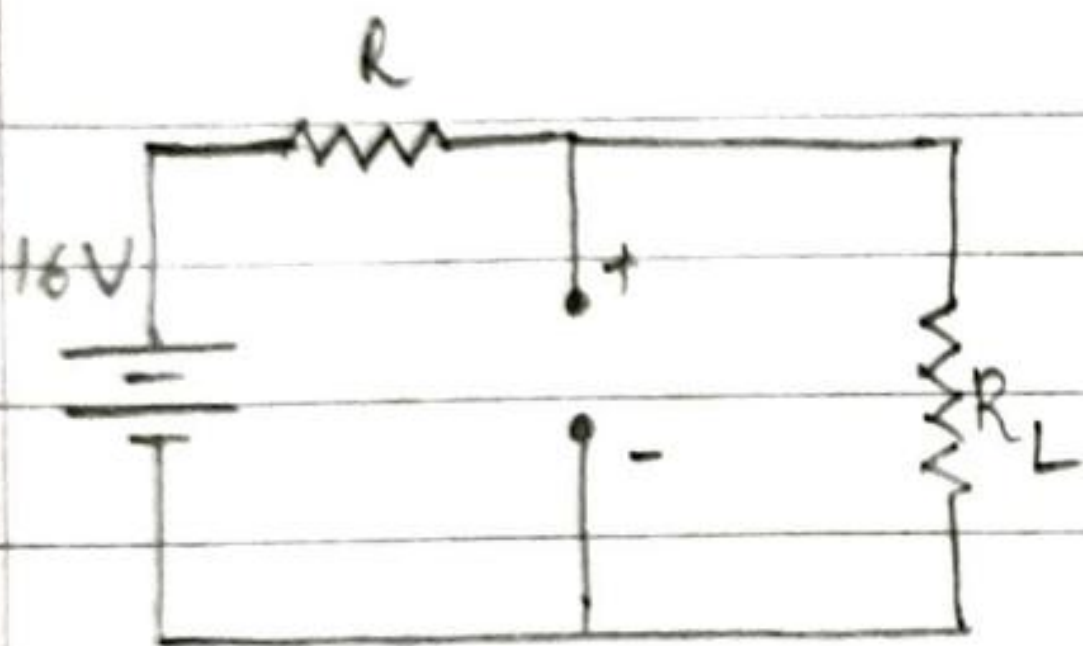This value is less than V_Z ($\because V_Z = 10V$) \therefore Zener is off. openckt.



$$V_L = V = 8.73V$$

$$V_R = V_i - V_Z = 16 - 8.73 = 7.27V$$


$$I_Z = 0 \text{ Amp.}$$

$$P_Z = V_Z \times I_Z = 0 \text{ Watts.}$$

(b) With $R_L = 3k\Omega$.

$$V = \frac{V_i \times R_L}{R_L + R} = \frac{16 \times 3k\Omega}{3k\Omega + 1k\Omega} = 12V$$

$12V > 10V \therefore$ Zener is ON.

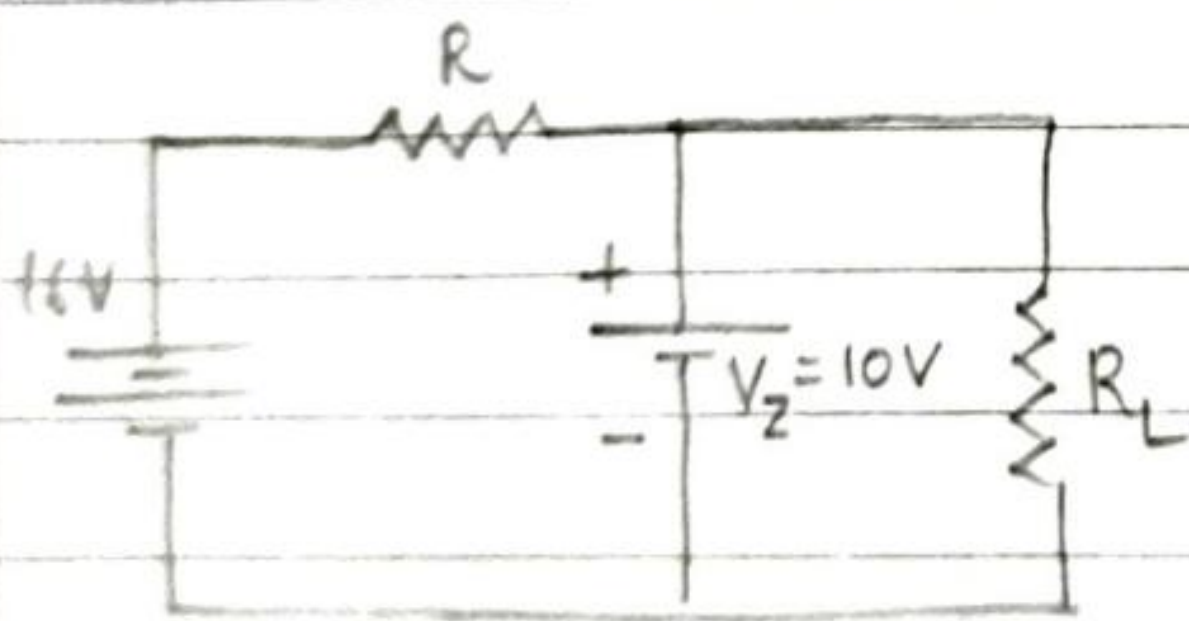

$$\therefore V_L = V_Z = 10V$$

$$V_R = \frac{V_i - V_Z}{R} = \frac{16 - 10}{1k\Omega} = 6mA$$

$$I_Z = I_R - I_L = 6mA - 3.33mA$$

$$= 2.67mA$$

$$P_Z = V_Z I_Z = 10 \times 2.67mA = 26.7mW (< 30mW)$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{3k\Omega} = 3.33mA$$

Q. A Zener diode is specified as having a breakdown voltage of 9.1V, with a max power dissipation of 364mW. What is the max current the diode can handle?

Soln:- $P_{ZM} = I_{ZM} \times V_Z$

$$\therefore I_{ZM} = \frac{P_{ZM}}{V_Z} = \frac{364mW}{9.1V} = \frac{364 \times 10^{-3}}{9.1} = 40mA$$

② FIXED V_i , VARIABLE R_L

- Due to the limited region (breakdown region) that the Zener diode can operate, there is a specific range of resistor values that ensures that Zener is in 'ON' state.
- Too small a load resistance ($V_L < V_Z$), I_L will be large, I_Z will fall by a large percentage & the Zener will be in 'OFF' state.
- Too large a load resistance, I_L will be negligible, max current will flow through Zener which might exceed I_{Zmax} .

To determine the minimum load resistance that will turn the Zener diode ON, we calculate the value of R_L that results in load voltage $V_L = V_Z$. That is,

$$V_L = V_Z = \frac{V_i \times R_{Lmin}}{R_{Lmin} + R}$$

$$\therefore V_Z (R_{Lmin} + R) = V_i \times R_{Lmin}$$

$$\therefore \boxed{R_{Lmin} = \frac{V_Z \times R}{V_i - V_Z}}$$

Any load resistance $> R_{Lmin}$ will ensure that Zener is in 'ON' state.

$$\therefore \boxed{I_{Lmax} = \frac{V_Z \text{ (or } V_L)}{R_{Lmin}}}$$

Once the diode is ON, $\boxed{V_R = V_i - V_Z}$ & $\boxed{I_R = \frac{V_R}{R}}$ fixed.

Zener current: $I_Z = I_R - I_L$


When I_L is min, max I_Z flows & when I_L is max, min I_Z flows thr' Zener. ($\because I_R$ is constant).

$$\therefore \boxed{I_{Lmin} = I_R - I_{ZM}}$$

* I_{Zmax} is written as I_{ZM} .

$$\therefore \boxed{R_{Lmax} = \frac{V_Z}{I_{Lmin}}}$$

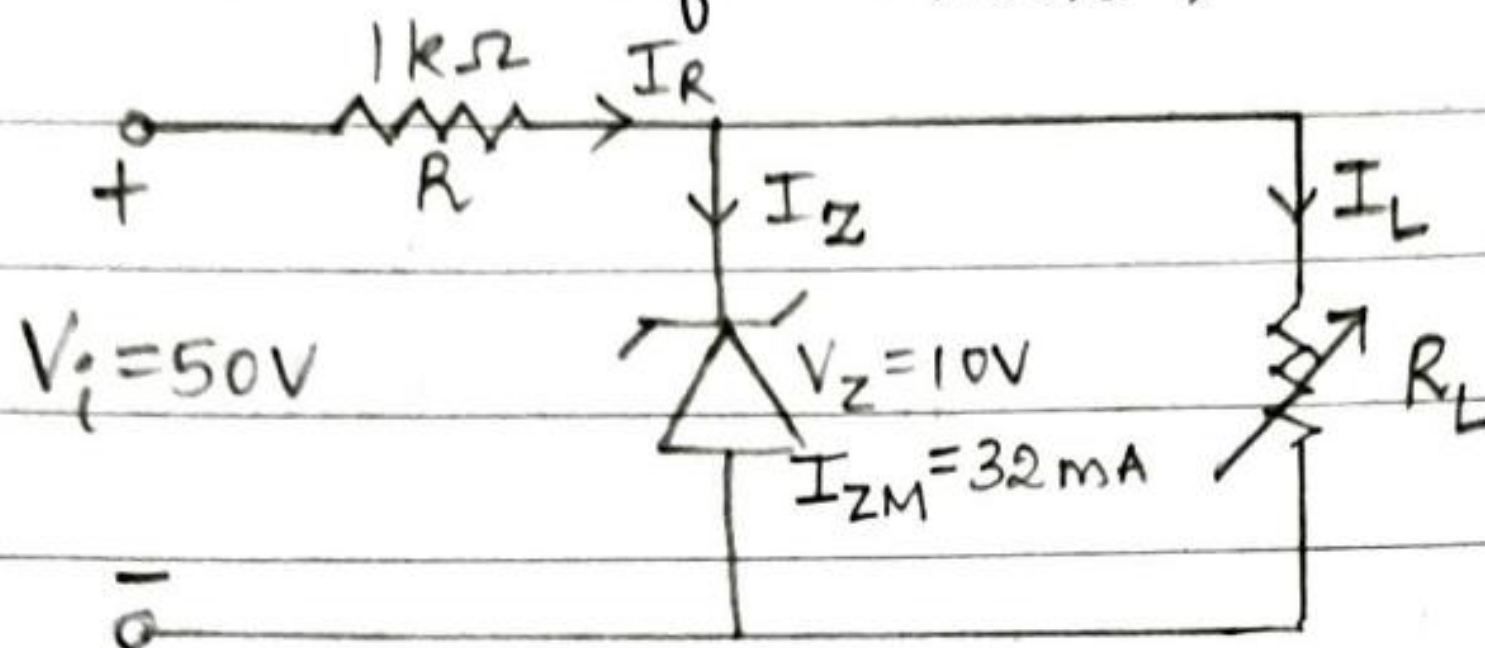- Q. For the given network (a) determine the range of R_L & I_L that will result in V_L being maintained at 10V.
 (b) Determine the maximum wattage rating of the diode.
 (c) If Zener max wattage is increased to 380 mW, what is the new value of I_{Lmin} ?



Soln:- (a) $R_{Lmin} = \frac{R V_Z}{V_i - V_Z}$
 $= \frac{1k \times 10}{50 - 10} = 250 \Omega$

$$V_R = V_i - V_Z = 50 - 10 = 40V$$

$$I_R = \frac{V_R}{R} = \frac{40}{1k} = 40mA$$

$$I_{Lmin} = I_R - I_{ZM} = 40mA - 32mA = 8mA$$

$$I_{Lmax} = \frac{V_Z}{R_{Lmin}} = \frac{10}{250} = 40mA$$

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}} = \frac{10}{8mA} = 1.25k\Omega$$

$$\therefore 250\Omega < R_L < 1.25k\Omega$$

$$8mA < I_L < 40mA$$

(b) $P_{Zmax} = I_{ZM} \times V_Z = 32mA \times 10V = 320mW$

(c) If $P_{Zmax(new)} = 380mW$

$$I_{ZM(new)} = \frac{P_{Zmax(new)}}{V_Z} = \frac{380mW}{10} = 38mA$$

$$\therefore \text{New value of } I_{Lmin} = I_R - I_{ZM(new)} = 40mA - 38mA = 2mA$$

③ FIXED R_L , VARIABLE V_i

For fixed values of R_L , V_i must be sufficiently large to turn the zener diode ON.

The minimum turn on voltage $V_{i\min}$ is determined by

$$V_L = V_Z = \frac{V_{i\min} \times R_L}{R + R_L}$$

$$\therefore \boxed{V_{i\min} = \frac{V_Z (R + R_L)}{R_L}}$$

I_L is fixed at $I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L}$


When I_R is max, maximum current flows thr' zener

$$\therefore \boxed{I_{R\max} = I_{ZM} + I_L}$$

Since $I_{R\max} = \frac{V_{i\max} - V_Z}{R} \Rightarrow \boxed{V_{i\max} = (I_{R\max} \times R) + V_Z}$

OR $\boxed{V_{i\max} = V_{R\max} + V_Z}$

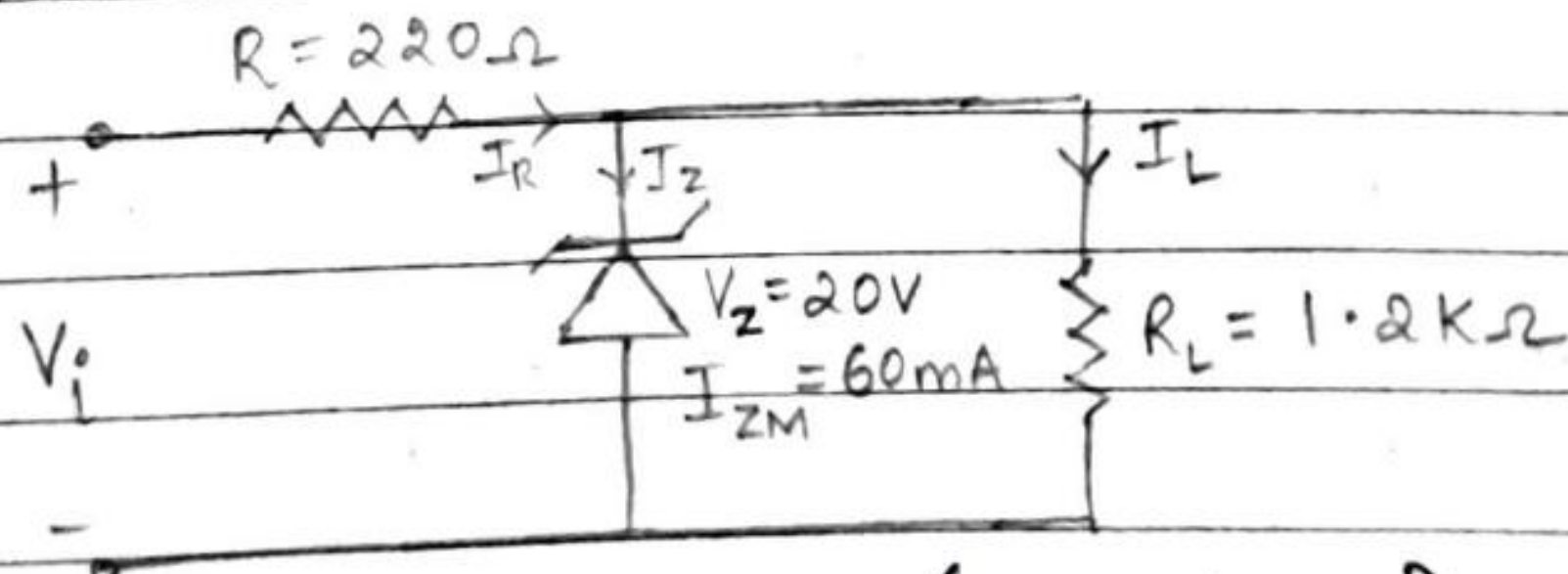Q. Determine the range of values of V_i that will maintain the zener diode in 'ON' state.



Soln:- $V_{i\min} = \frac{V_Z (R_L + R)}{R_L} = \frac{20(1.2K + 220)}{1.2K} = 23.67 \text{ V}$

$$I_L = \frac{V_L}{R_L} = \frac{V_Z}{R_L} = \frac{20 \text{ V}}{1.2 \text{ K}} = 16.67 \text{ mA}$$


$$I_{R\max} = I_{ZM} + I_L = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$

$$V_{i\max} = I_{R\max} R + V_Z = (76.67 \text{ mA} \times 220) + 20 = 36.87 \text{ V}$$

$$\therefore 23.67 \text{ V} < V_i < 36.87 \text{ V}$$

Problems.

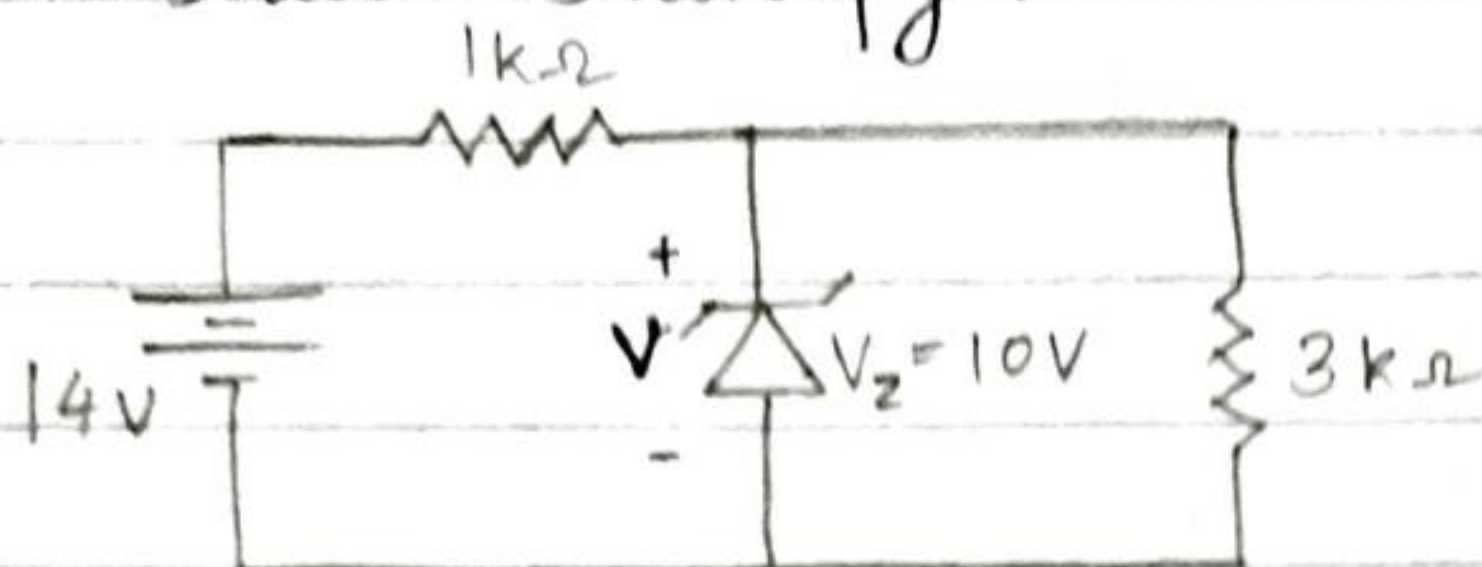
Q1) In the ckt shown, is the zener diode in 'ON' state or 'OFF' state. Justify.



Soln:
$$V = \frac{V_z \times R_L}{R_L + R}$$
$$= \frac{14 \times 3k\Omega}{3k\Omega + 1k\Omega} = 10.5 \text{ V}$$

$\therefore V > V_z \therefore$ Zener is in ON state.

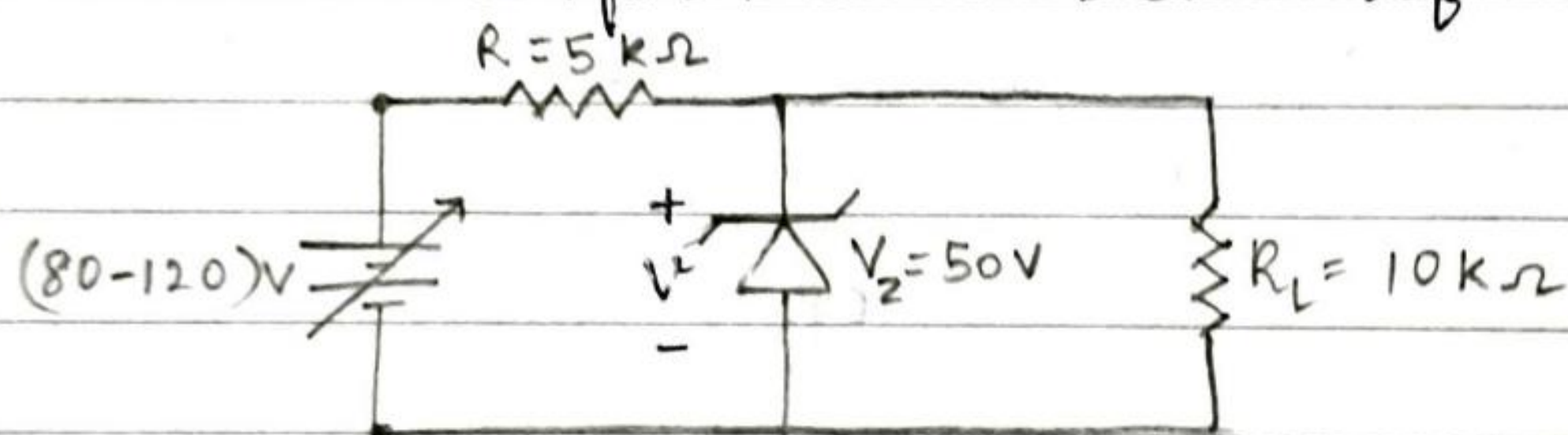★★ Q2) Determine maximum & minimum values of zener diode current for the ckt below if $V_z = 50 \text{ V}$.



Soln: $- V_i$ varies from 80V to 120V.

To ensure zener is in ON state for this entire range, atleast V_{imin} (i.e 80V) should be enough to turn it ON.

$$V = \frac{V_i \times R_L}{R_L + R} = \frac{80 \times 10k\Omega}{10k\Omega + 5k\Omega} = 53.33 \text{ V}$$

$\therefore V > V_z \therefore$ Zener is always in ON state.

(i) Consider $V_{imin} = 80 \text{ V}$

$$I_{R_{min}} = \frac{V_R}{R} = \frac{V_{imin} - V_z}{R} = \frac{80 - 50}{5k\Omega} = 6 \text{ mA}$$

$$I_L = \frac{V_z}{R_L} = \frac{50}{10k\Omega} = 5 \text{ mA}$$

$$\therefore I_{zmin} = I_{Rmin} - I_L = 6 \text{ mA} - 5 \text{ mA} = 1 \text{ mA}$$


(ii) Consider $V_{imax} = 120 \text{ V}$

$$I_{Rmax} = \frac{V_{imax} - V_z}{R} = \frac{120 - 50}{5k\Omega} = 14 \text{ mA}$$

$$\therefore I_{Z_{\max}} = I_{R_{\max}} - I_L = 14 \text{ mA} - 5 \text{ mA} = \underline{9 \text{ mA}}$$

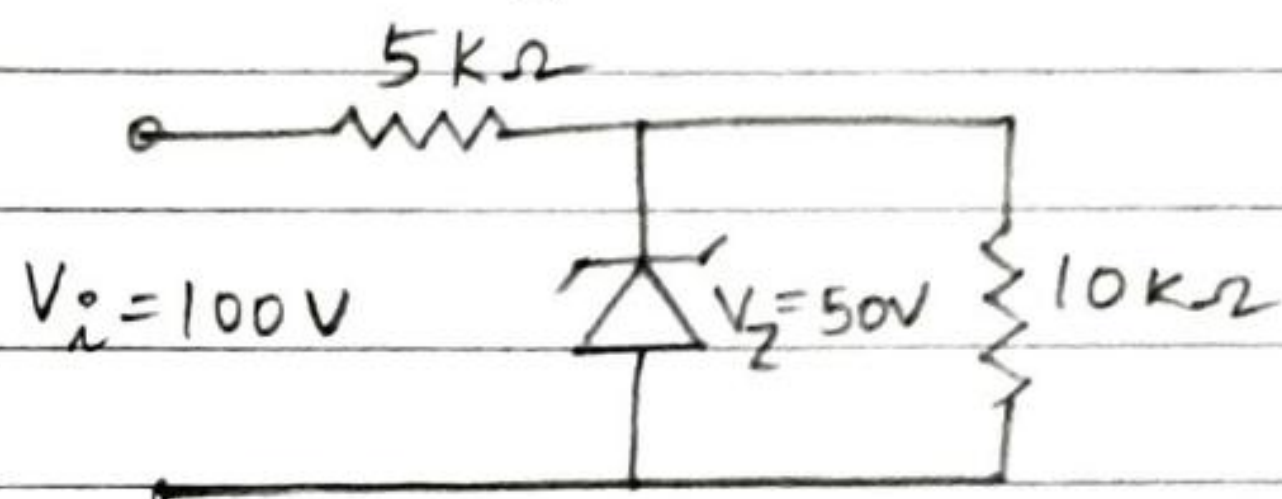Q3) For the circuit shown, find the voltage drop across $5 \text{ k}\Omega$ resistance.

Soln: Step 1: Make sure zener is in 'ON' state



$$V = \frac{V_i \times R_L}{R_L + R} = \frac{100 \times 10 \text{ k}\Omega}{15 \text{ k}\Omega} = 66.67 \text{ V}$$


$\therefore V > V_Z \therefore$ Zener diode is in ON state $\therefore V_L = V_Z = 50 \text{ V}$.

$$\therefore V_R = V_i - V_Z = 100 - 50 = \underline{50 \text{ V}}$$

* Q4) For the ckt shown, determine:-

(a) V_L , I_L , I_Z & I_R with $R_L = 200 \Omega$

(b) Repeat with $R_L = 50 \Omega$.

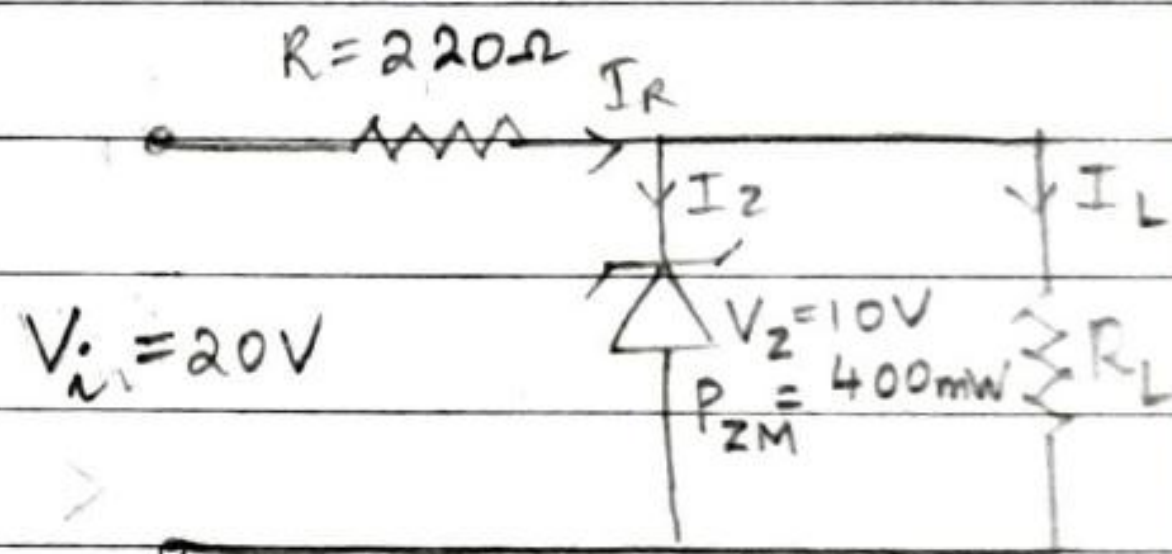

Soln: (a) For $R_L = 200 \Omega$.

* check first for zener state

$$V = \frac{V_i R_L}{R_L + R} = \frac{20 \times 200}{200 + 220} = 9.524 \text{ V}$$

$V < V_Z \therefore$ Zener is in OFF state (open circuit)

$$\therefore V_L = 9.524 \text{ V}, \quad I_Z = 0 \text{ Amp}$$

$$I_L = I_R = \frac{V_i}{R + R_L} = \frac{20}{220 + 200} = 47.62 \text{ mA}$$

(b) For $R_L = 50 \Omega$


* Check for zener state

$$V = \frac{V_i \times R_L}{R + R_L} = \frac{20 \times 50}{50 + 220} = 3.7 \text{ V} \therefore \text{Zener is OFF (o.c.)}$$

$$V_L = 3.7 \text{ V}, \quad I_Z = 0 \text{ Amp}$$

$$I_L = I_R = \frac{V_i}{R_L + R} = \frac{20}{220 + 50} = 74.07 \text{ mA}$$

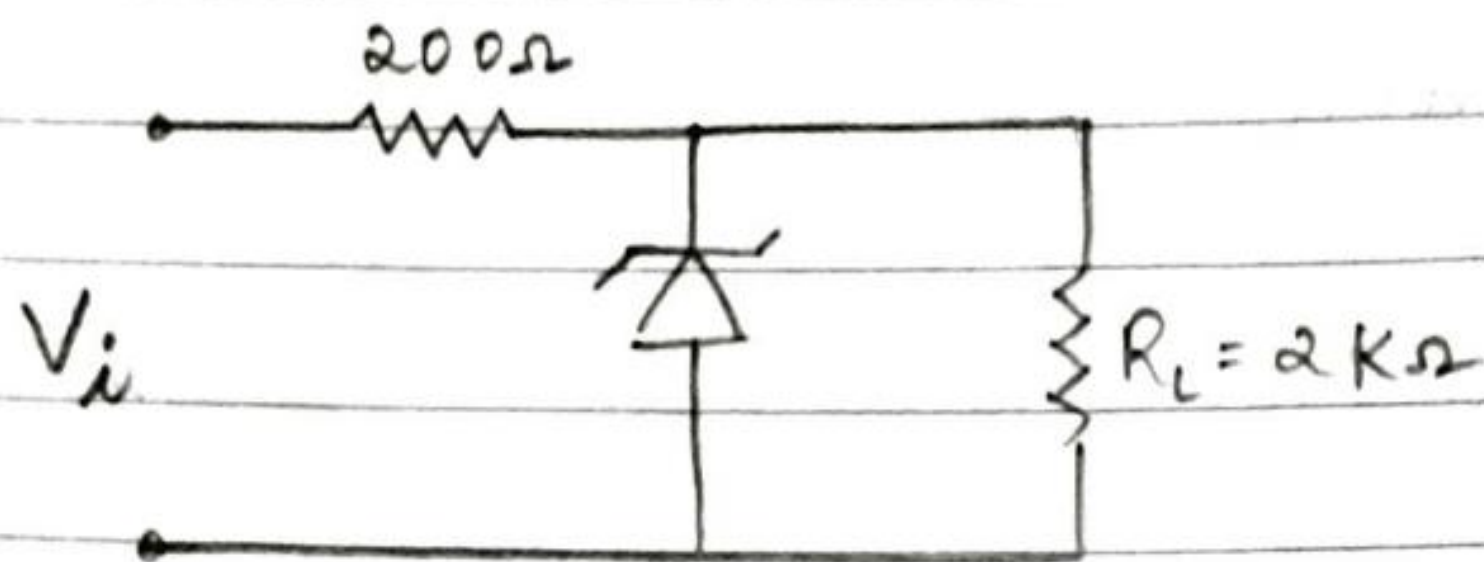- ★ Q5) Over what range of i/p voltage will the zener ckt shown maintain 30V across the 2k Ω load assuming that series resistance $R=200\Omega$ & Zener current rating = 25mA.



Soln :- Given $V_Z = 30V$ & $I_{ZM} = 25mA$.


$$V_{i_{min}} = \frac{V_Z(R_L + R)}{R_L} = \frac{30(2k + 200)}{2k} = 33V$$

$$\begin{aligned} I_{R_{max}} &= I_{ZM} + I_L \\ &= 25mA + 15mA \quad \left(\because I_L = \frac{V_L}{R_L} = \frac{30}{2k} = 15mA \right) \\ &= 40mA \end{aligned}$$

$$\begin{aligned} V_{i_{max}} &= (I_{R_{max}} \times R) + V_Z \\ &= (40mA \times 200) + 30 = 38V \end{aligned}$$

$$\therefore 33V < V_i < 38V$$

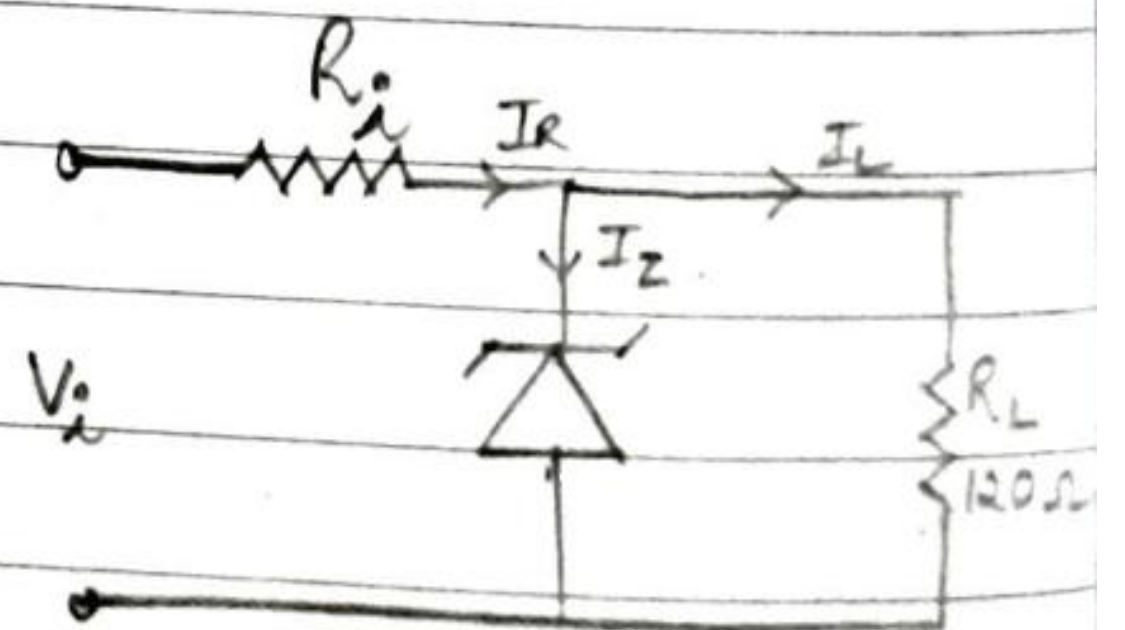- ★ Q6) The zener diode regulator ckt, has a fixed voltage drop of 12V across it as long as I_Z is maintained between 20mA to 200mA. Find R_i so that V_L remains at 12V while V_i varies from 15V to 19.5V.



Soln :- I_L is fixed, Since R_L is fixed

$$\therefore I_L = \frac{V_L}{R_L} = \frac{12}{120} = 100mA$$

For $V_{i_{min}} = 15V$

$$V_{R(min)} = V_{i_{min}} - V_Z = 15 - 12 = 3V$$

For $V_{i\max} = 19.5\text{V}$

$$V_{R(\max)} = V_{i\max} - V_Z = 19.5 - 12 = 7.5\text{V}$$

Now, $I_{R\min} = I_{Z\min} + I_L = 20\text{mA} + 100\text{mA} = 120\text{mA}$

& $I_{R\max} = I_{Z\max} + I_L = 200\text{mA} + 100\text{mA} = 300\text{mA}$

$$\therefore R_i = \frac{V_{R\min}}{I_{R\min}}$$

$$= \frac{3\text{V}}{120\text{mA}}$$

$$= 25\Omega$$

OR


$$R_i = \frac{V_{R\max}}{I_{R\max}}$$

$$= \frac{7.5\text{V}}{300\text{mA}}$$

$$= 25\Omega$$

$$\therefore R_i = 25\Omega$$

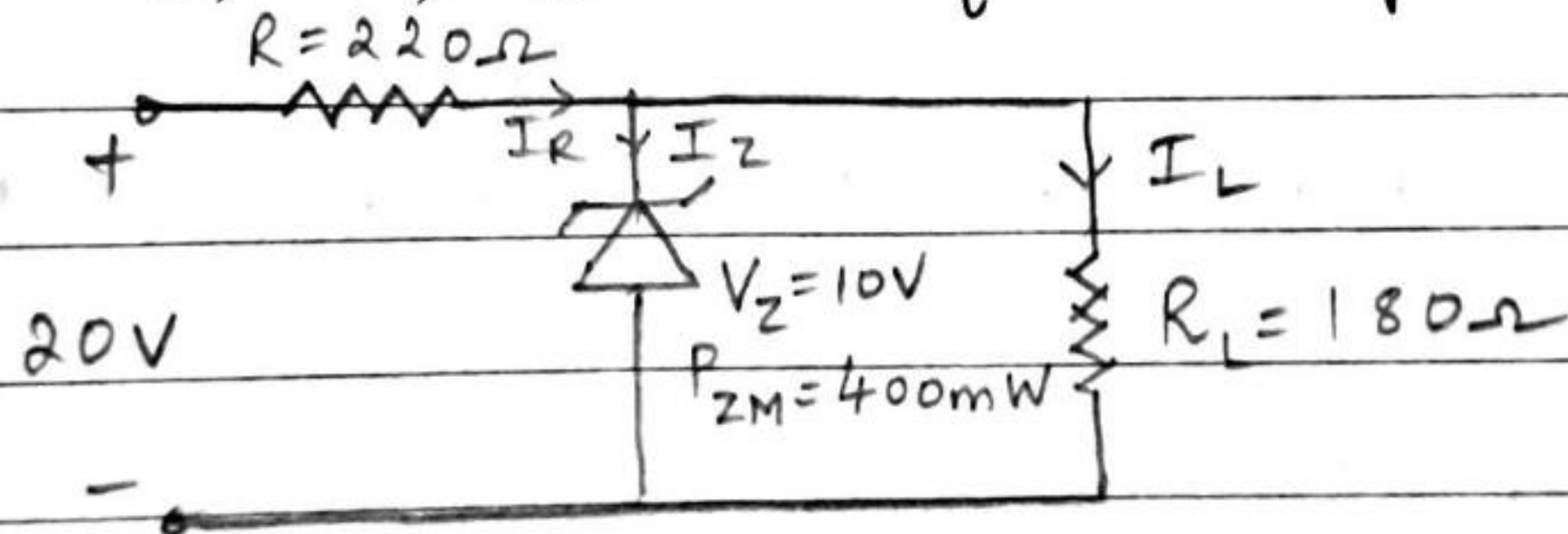Q7) Determine V_L , I_L , I_R & I_Z for the foll n/w if $R_L = 180\Omega$.



Solⁿ: Check state of zener:

$$V = \frac{V_i \times R_L}{R_L + R} = \frac{20 \times 180}{180 + 220} = 9\text{V} < V_Z$$

\therefore Zener is OFF

$$V_L = V = 9\text{V}$$

$$I_L = \frac{V_L}{R_L} = \frac{9}{180} = 50\text{mA}$$

$$I_Z = 0\text{Amp}$$

$$I_R = I_L = 50\text{mA}$$

$$\left[I_R = \frac{V_R}{R} = \frac{20-9}{220} = 50\text{mA} \right]$$

More Problems: Sedha Pg 470