



SEM 1-4 (RC 2016-17)

F.E. Semester – I (RC 2016-17) Examination, Nov./Dec. 2016 FUNDAMENTALS OF ELECTRICAL ENGINEERING (New)

Duration : 3 Hours

Total Marks : 100

- Instructions :**
- 1) Answer **any two** questions from Part – A.
 - 2) Answer **any two** questions from Part – B.
 - 3) Answer **any one** question from Part – C.
 - 4) **Assume** suitable data, if required.

PART – A

1. a) Explain with the help of schematic/Block diagram the working of a thermal power plant. 8
- b) Draw a single line diagram representing electrical power system. Write typical values of voltages at different levels. 7
- c) When one coil of a magnetically coupled pair has a current 5A the resulting fluxes ϕ_{11} and ϕ_{12} are 0.2 mWb and 0.4mWb, respectively. If the turns are 500 and 1500, find L_1 , L_2 , M and coefficient of coupling K. 5
2. a) Define the following terms : 4
 - i) Ideal and practical current source
 - ii) Planar circuits.
- b) Using superposition theorem find the current i_y in the circuit of fig. 2(b)

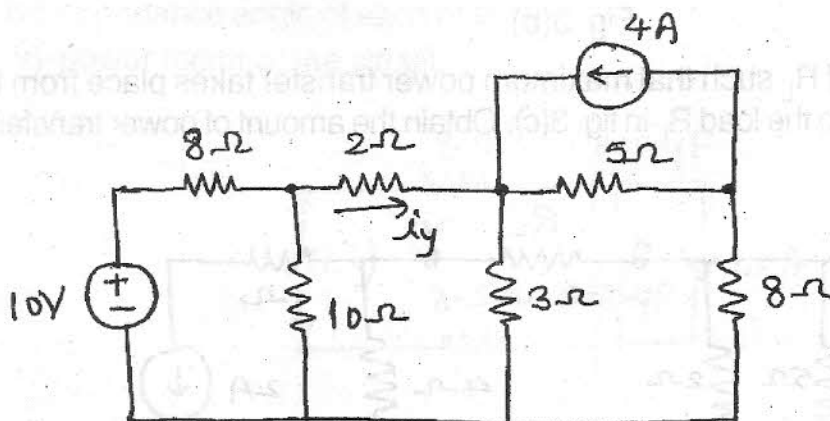


Fig.2(b)

P.T.O.



- c) Thevenize the bridge circuit across a – b in fig. 2(c).

8

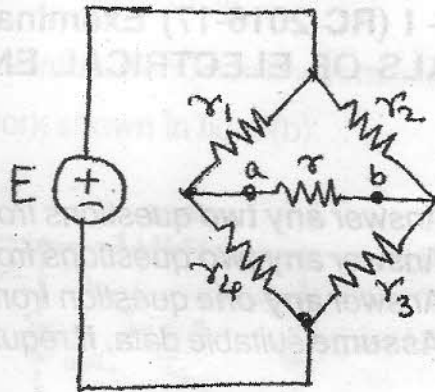


Fig.2(c)

3. a) State and explain Norton's theorem.
 b) In the fig. 3(b), let $L_1 = 0.4 \text{ H}$; $L_2 = 2.5 \text{ H}$; $K = 0.6$ and $i_1 = 4$, $i_2 = 20 \cos(500t - 20^\circ) \text{ mA}$. Evaluate the following quantities at $t = 0$.
 1) i_2
 2) v_1
 3) The total energy stored in the system.

4

8

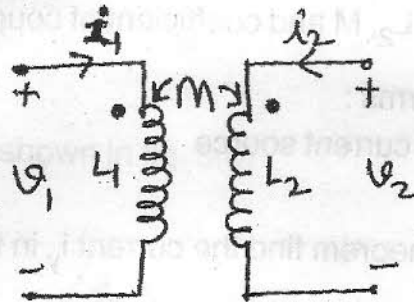


Fig. 3(b)

- c) Find the value of R_L such that maximum power transfer takes place from the current sources to the load R_L in fig. 3(c). Obtain the amount of power transfer.

8

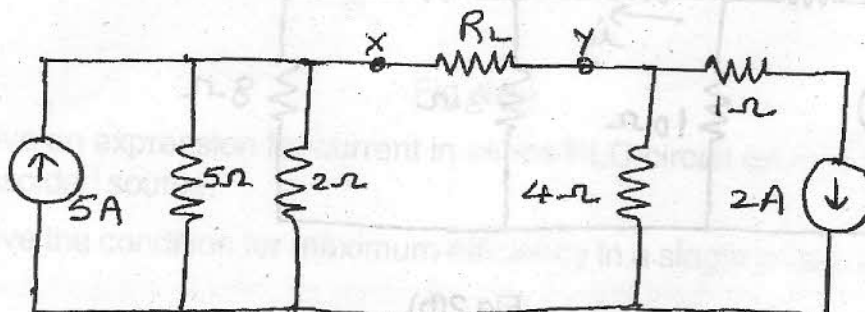


Fig. 3(c)



PART – B

4. a) Define the following terms :
i) Average value
ii) Form factor
iii) Active power
iv) Power factor. 8
- b) A 4 ohm resistor is connected to a 10 mH inductor a 100 V, 50Hz voltage source. Find
i) Power factor of the circuit
ii) Total power supplied. 4
- c) A 10Ω resistor is connected in parallel with a $100\mu\text{F}$ capacitor. Supply being 5A, 50 Hz current source, find the rms and instantaneous branch currents through the capacitor and resistor. 8
5. a) Is three phase system preferred over single phase system ? Why ? 6
b) Explain the working of a single phase transformer. 6
c) Three similar coils, each having a resistance of 3Ω and an inductive reactance of 4Ω are connected in i) Y and ii) Δ , across a 400 V, three-phase supply. Calculate for each connection the readings on each of the two wattmeters connected to measure the power by the two-wattmeters method. 8
6. a) In the circuit shown in fig. 6(a) if the supply frequency is 60 Hz, find :
i) drop across each circuit element
ii) total resistive and capacitive drop
iii) supply voltage
iv) impedance angle of each branch
v) power factor of the circuit. 10

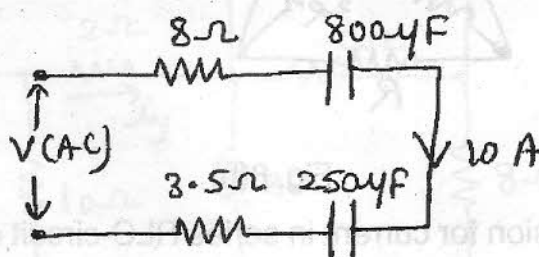


Fig. 6(a)

- b) Explain how the various losses and efficiency of a single phase transformer are measured/calculated without loading the transformer. 10



PART – C

7. a) Differentiate between conventional and non conventional sources of energy. 5
 b) Find current I in the network shown in fig. 7(b). 5

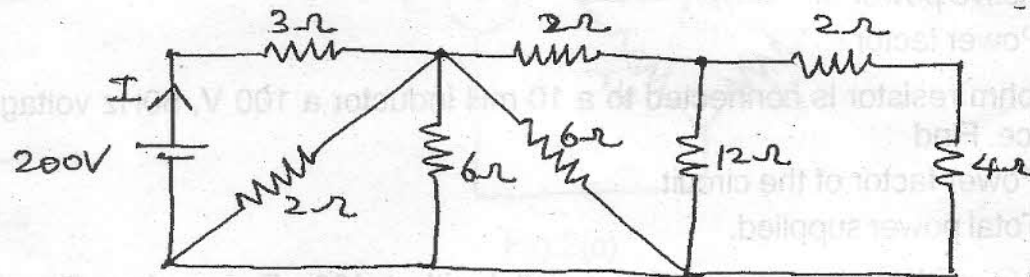


Fig. 7(b)

- c) A coil takes current of $1\angle 60^\circ$ A (lag) from 100 V, 60 Hz, supply. Calculate its inductances, resistance and impedance. 6
 d) Draw the equivalent circuit of a transformer. 4
8. a) Define the following terms :
 i) Reluctance
 ii) Ampere's law. 4
- b) Find R_{xy} in the circuit shown in fig. 8(b) 5

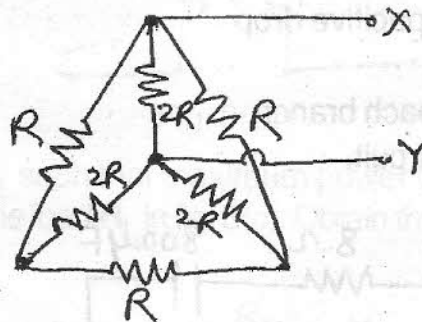


Fig. 8(b)

- c) Derive an expression for current in series RLC-circuit excited from a sinusoidal source. 6
 d) Derive the condition for maximum efficiency in a single phase transformer. 5