



PADRE CONCEIÇÃO COLLEGE OF ENGINEERING

Verna - Goa

Department of Electronics and Telecommunication Engineering

Roll No:

--	--	--	--	--	--

Internal Test-I

Semester & Course: I (RC 2019)

Course: FE130 Basic Electrical and Electronics Engineering



Course Instructor: Shivani Lotlikar (Chemistry Group)

Date: 09/01/2021

Time: 10:00 am- 12:00 noon

Max Marks: 25

Instructions: All questions are compulsory. Assume missing data, if any and justify.
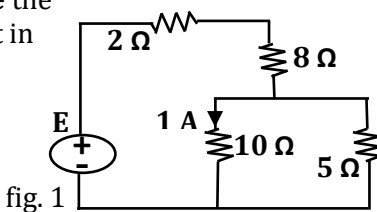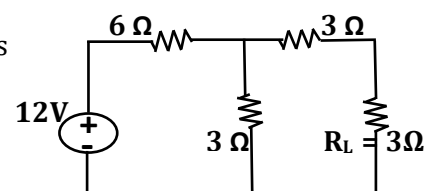
<u>Q. No</u>	<u>Questions</u>	<u>Marks</u>	<u>CO</u>	<u>CL</u>
Q1. a.	State Kirchhoff's laws.	[2]	FE130.1	CL1
b.	Compare the electric and magnetic circuit.	[3]	FE130.1	CL2
Q2.	Explain the following : i) Faraday's Law of Electromagnetic induction ii) Ampere's Law iii) Reluctance in magnetic circuit iv) Leakage flux.	[5]	FE130.1	CL2
Q3.	In the circuit given in fig. 1 determine the value of the emf source E if the current in 10Ω resistor is 1 A.	[5]	FE130.2	CL3
 <p>fig. 1</p>				
Q4. a.	State the Superposition Theorem.	[1]	FE130.2	CL1
b.	In the circuit given in fig. 2 determine the current in $R_L = 3\Omega$ using Thevenin's theorem.	[4]	FE130.2	CL3
 <p>fig. 2</p>				
Q5.a.	Draw a neat labelled V-I characteristics of a p-n junction diode. And explain the following: (i) Knee Voltage (ii) Reverse Breakdown Voltage	[3]	FE130.3	CL2
b.	Differentiate between avalanche breakdown and zener breakdown.	[2]	FE130.3	CL2

.....